



INDIAN SCHOOL AL WADI AL KABIR

Class: XI	Department: Computer Science	Date of submission: 06/05/2021
Worksheet -3	Topic: Boolean Algebra	Note: for practice

1. Prove the Boolean Laws shown below using Truth Table.

1. $X + X'Y = X + Y$
2. $X + XY = X$
3. $X + YZ = (X + Y)(X + Z)$

2. Write a short note on Boolean Algebra.

3. State and prove absorption law and involution law.

4. State and prove De Morgan's Theorems.


- i. Use truth table
- ii. Use algebraic method

5. State and prove complementarity law .Use algebraic method to prove it .


6.State and prove idempotence law. Use algebraic method to prove it.

7. Convert the following logic gate circuit into a Boolean expression.(Write the Boolean expression for the given circuits)


1.

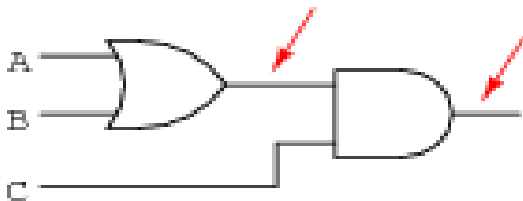

2.

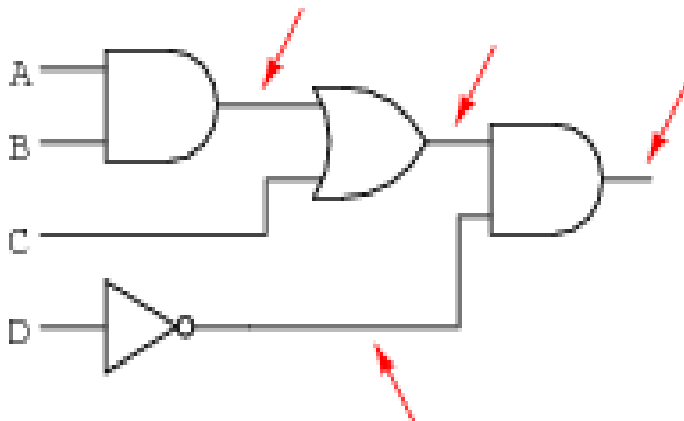

3.

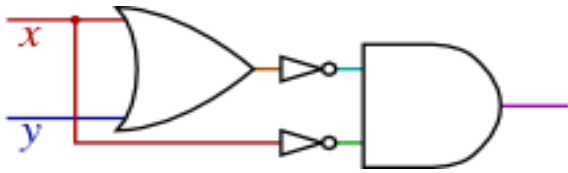

8.

1. Draw Logic circuit for $y = A.C + B.C' + A'.B.C$

2. Draw Boolean Logical Circuit from the given Boolean expression:

$$Q = A.B + B.C.(B+C)$$

3. Draw Logic circuit for $y = A.C + B.C' + A'.B.C$

4. Draw a circuit diagram corresponding to the following Boolean Expression:

a) $y = A+C .B+C' . A'+B+C$

b) $F = A'.B.C.(A+D)'$


c) $F = A.B'+C'.D$

d) $F = (U.V')+(U'.W')$

e) $F = A.B + A.C' + B'.A'.C$

f) $F = (X+Y).(X'+Z).(Y+Z)$

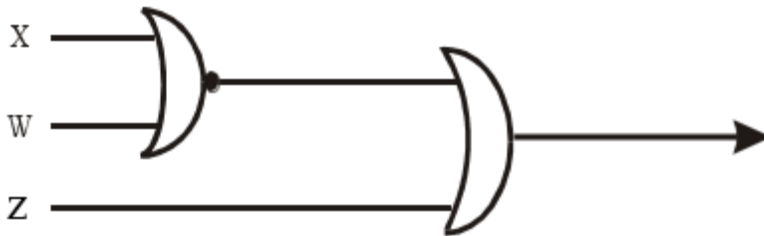9. Obtain logic expression for the following logic circuit:



10.

(a) Verify the following using Boolean Laws :

$$A' + B'.C = A'.B'.C' + A'.B.C' + A'.B.C + A'.B'.C + A.B'.C$$

(b) Write the Boolean Expression for the result of the Logic Circuit as shown below :

